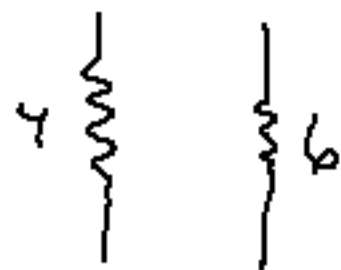


$$R_T = 2.4 \Omega$$



	<u>I</u>	<u>V</u>
$R_1: 4 \Omega$	2A	8V
$R_2: 2 \Omega$	2A	4V
$R_3: 4 \Omega$	3A	12V

$$V = IR$$

$$12 = I(4)$$

$$3 = I$$


$$V = IR$$

$$12 = I(2.4)$$

$$5 = I$$

$$V = 2(4)$$

$$V = 2(2)$$

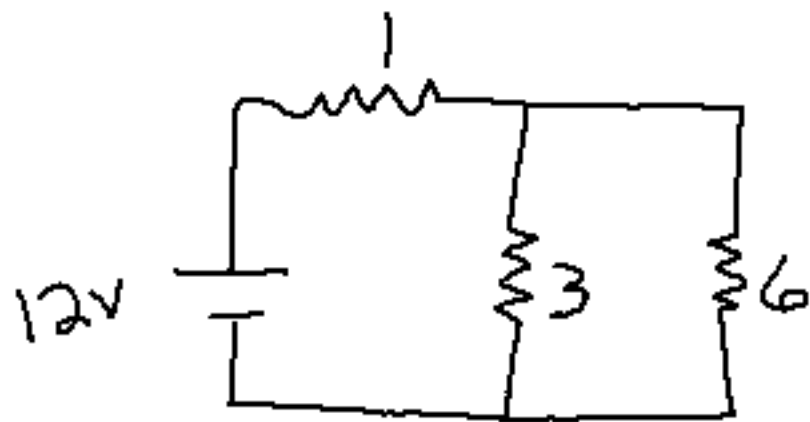

$$R_T = 3 \Omega$$

$$12 = I_3$$

$$4A = I$$

$$I_T = 4A$$

$$1 \Omega: \frac{V}{4A} \quad \frac{I}{4A} \quad V = 4(1)$$



$$3 \Omega: 8V \quad \frac{8}{3} = 2.67A \quad 8 = I_3$$

$$6 \Omega: 8V \quad \frac{8}{6} = 1.33A \quad 8 = I_6$$

$$\frac{4}{3} = I$$

p 528 figure 19-10

Worksheet - Sample Problem.

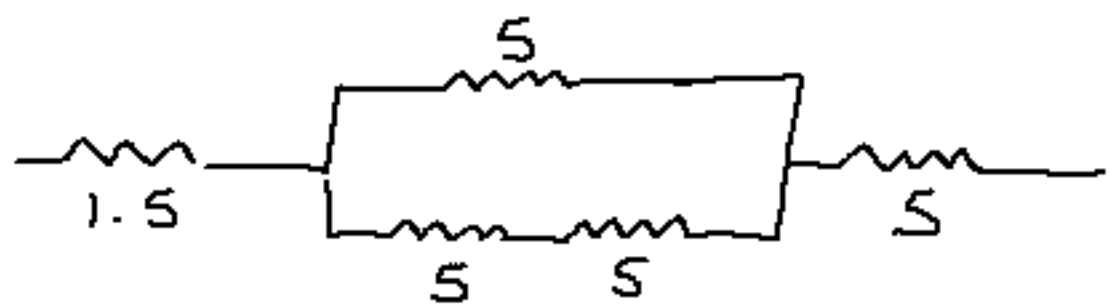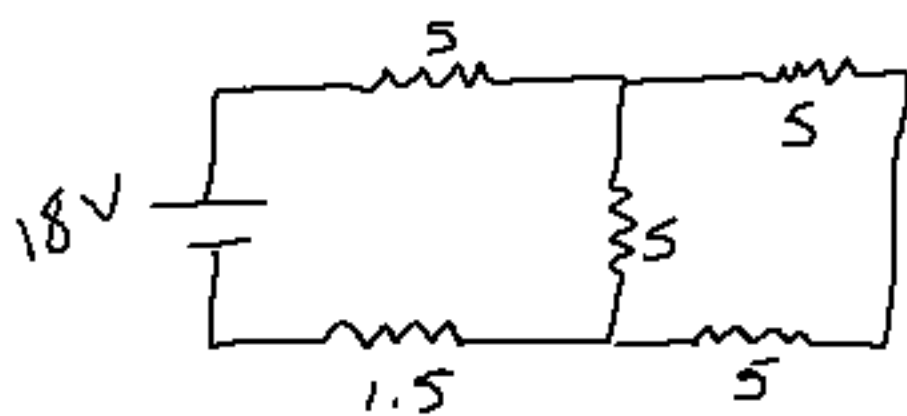

①  $R_T = 9.83$

$V = IR$


$18 = I(9.83)$

②  $1.83A = I$

③  $V = IR$   
 $= 1.83(1.5)$

$V = 2.75V$

43

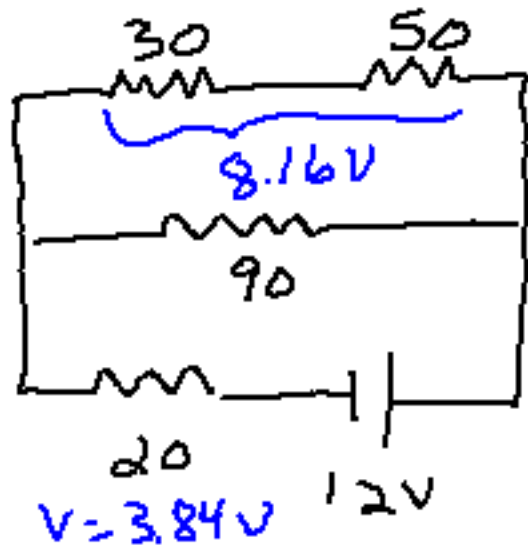


a)  $R_T = 62.4 \Omega$

b) Total current

$$12 = I 62.4$$

$$.192 A = I$$

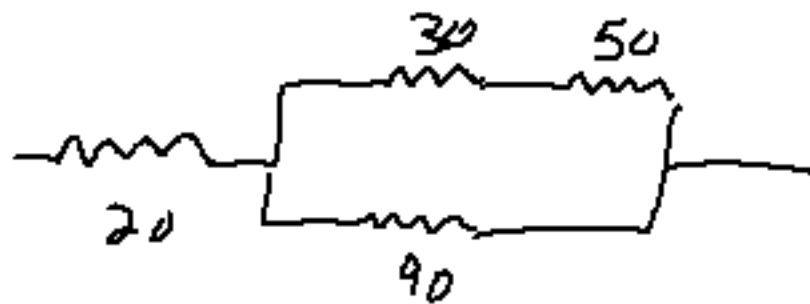

$$20 \Omega : I = .192$$

$$V = .192(20)$$



$$V = 3.84 V$$

$$V = IR$$

$$8.16 = I 80$$

$$.102 A = I$$

$$V = i/c$$

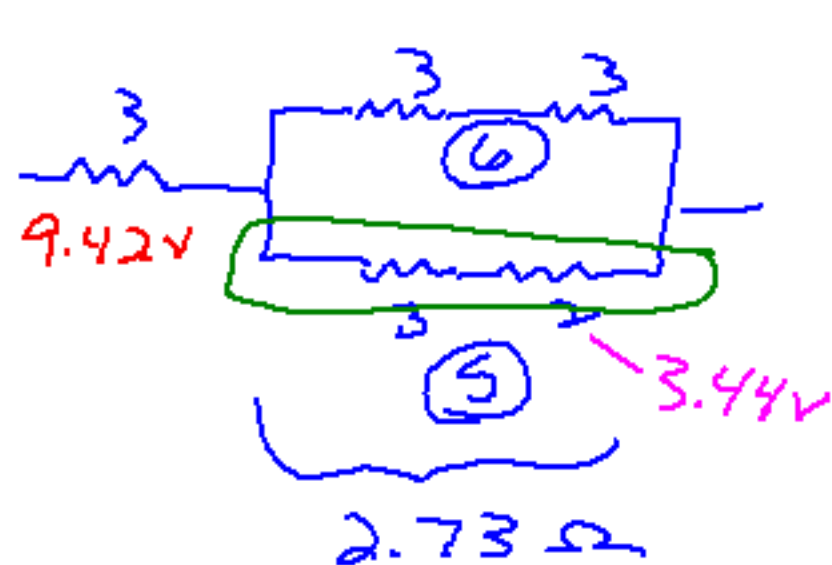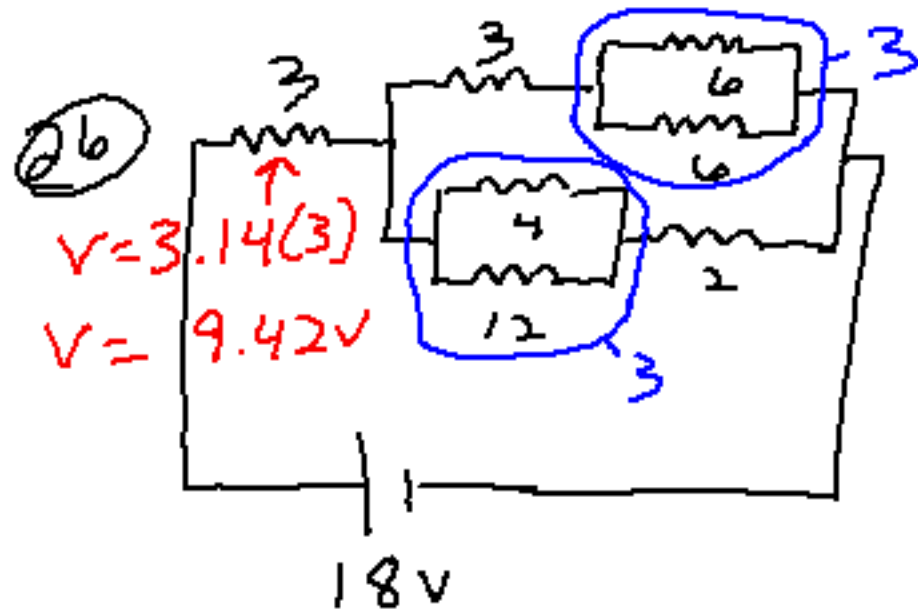

$$18 - 9.42 = 8.58V$$

$$V = IR$$

$$8.58 = I 5$$

$$(a) 1.72A = I$$

$$(b) V = 1.72(2) = 3.44V$$

$$(c) 8.58 - 3.44 = 5.14V$$

$$(d) 5.14 = I 12$$


$$I = .428A$$

$$R_T = 5.73$$

$$V = IR$$

$$18 = I 5.73$$

$$I = 3.14A$$

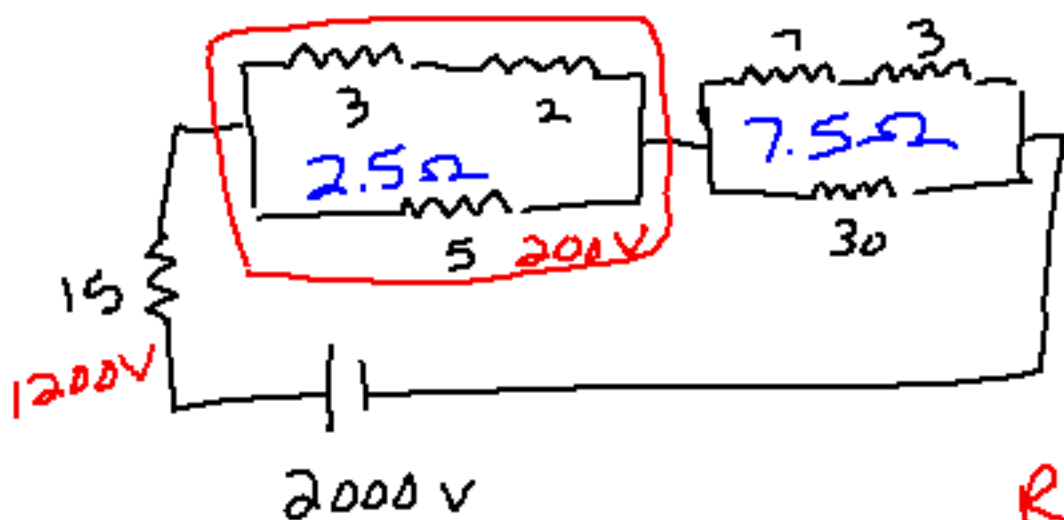

$$R_T = 25 \Omega$$

$$V = IR$$

$$2000 = I(25)$$

$$80A = I$$

$$V = 80(15) = 1200V$$

$$R = 2.5 \Omega$$

$$I = 80A$$

$$V = IR$$

$$(a) V = 80(2.5) = 200V$$

$$V = IR$$

$$200 = I(5)$$

$$I = 40A$$

$$(a) 600V$$

$$600 = I(30)$$

$$20A = I$$

1<sup>st</sup> sheet.

# 25,46

2<sup>nd</sup> sheet

one at bottom.